

Single-Phase Full-Bridge Inverter

Module 6 – Power Electronics Laboratory

Toias Lozano, Santiago Ibarra, Rafael Ramos

Project Context

This module focuses on building a low-power single-phase full-bridge inverter using:


- Arduino-generated SPWM signals,
- IR2110 high/low-side drivers,
- Four N-channel MOSFETs in a full H-bridge.

The goal was to convert a 12 V DC supply into a 120 V AC-shaped waveform using unfiltered SPWM. The implementation followed the reference design exactly.

What is a Full-Bridge Inverter?

A full-bridge inverter is an electronic converter that transforms DC power into AC by switching four power transistors in an H configuration.

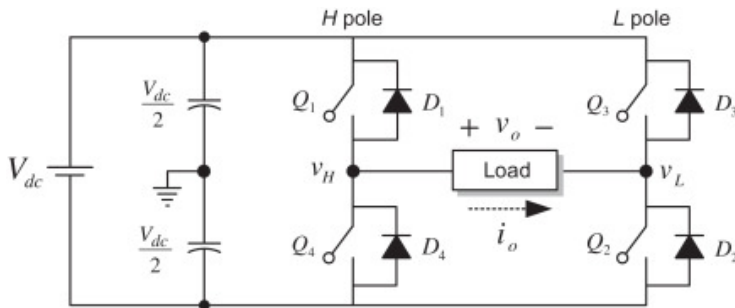- Can generate positive and negative output voltages.
- Forms the basis of UPS systems, motor drives, and renewable energy inverters.
- The output waveform depends on the modulation strategy.



General Operation

The circuit operates by switching MOSFET pairs:


- One pair produces the positive half-cycle.
- The opposite pair produces the negative half-cycle.

The Arduino controls this switching through SPWM pulses whose width follows a sinusoidal pattern, creating an AC waveform from a DC supply.

Sinusoidal PWM (SPWM)

SPWM adjusts the width of each pulse to approximate a sine wave.

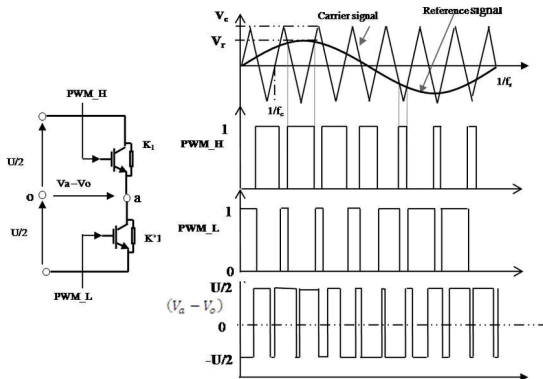
- Simple, efficient, widely used in power electronics.
- Arduino generates two complementary SPWM outputs.
- The output load receives a high-frequency pulse train whose envelope resembles a sine wave.



Arduino Uno

The Arduino Uno acts as the SPWM generator.

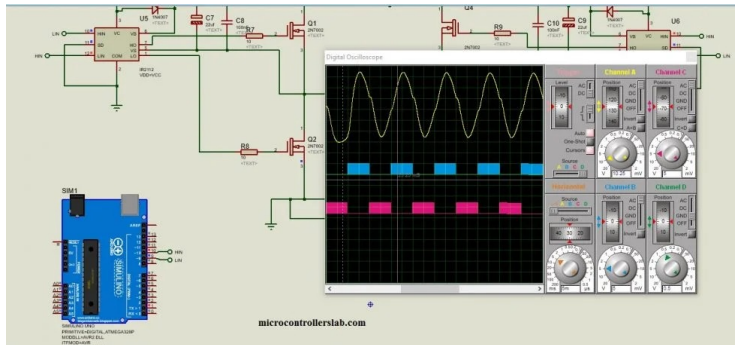
- Produces the pulse sequence for both half-cycles.
- Provides timing control.
- Includes a start-up delay to avoid undefined states.



IR2110 Gate Driver

The IR2110 allows an Arduino (5 V logic) to control MOSFETs on both low- and high-side positions.

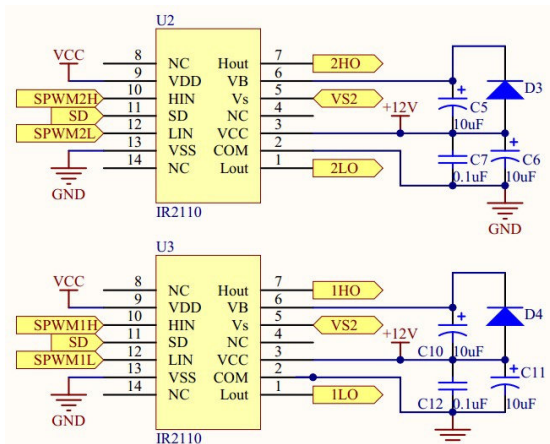
- Provides proper gate voltage levels.
- Uses bootstrap capacitors for high-side MOSFETs.
- Ensures fast and safe switching.



MOSFET H-Bridge

Four N-channel MOSFETs form the full H-bridge:

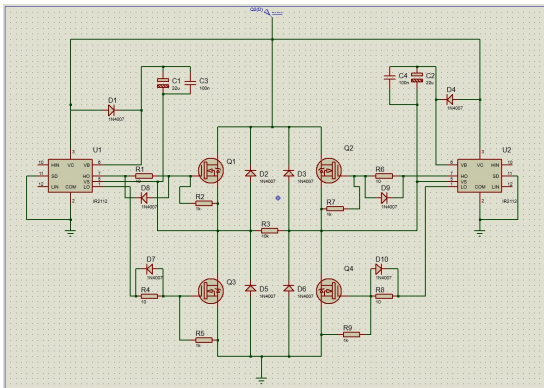- High efficiency
- Low conduction losses
- Provide the AC polarity reversal



Materials Used

Control and Drivers

- Arduino Uno R3
- IR2110 drivers ($2\times$)
- Bootstrap capacitor + diode network


Power Stage

- 4 MOSFETs (IRF3205 or equivalent)
- 150 Ω gate resistors
- 1 k pull-down resistors


Equipment

- 12.4 V bench supply
- Oscilloscope, multimeter

Laboratory

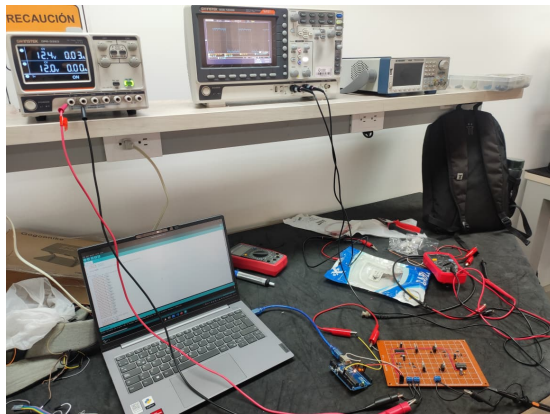

Laboratory Setup

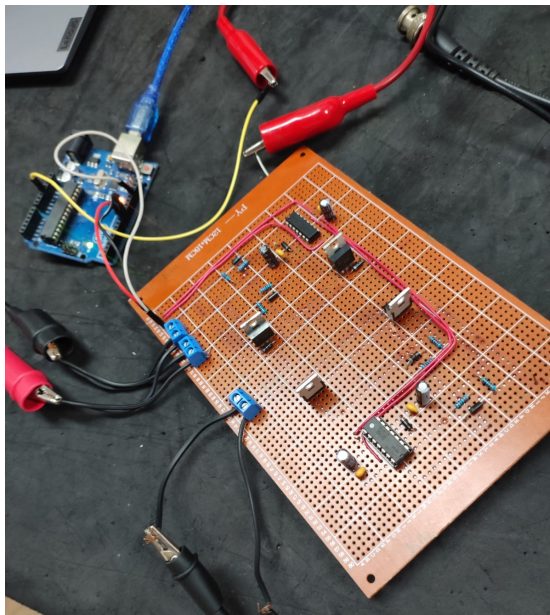

Observations

- Correct SPWM signals at Arduino outputs.
- IR2110 showed stable high/low-side operation.
- MOSFETs switched without cross-conduction.
- Output waveform matched simulation and theory.
- Supply during tests: approx. 12.4 V.

The full-bridge inverter prototype worked as expected. SPWM modulation successfully produced the pseudo-sinusoidal output, and the driver stage operated reliably.

Future improvements:

- Add LC filtering
- Implement feedback control
- Power the inverter from a rectifier stage

References

- Rashid, M. H. (2017). *Power electronics: Devices, circuits, and applications*. Pearson.
- Swagatam. (2025). Arduino H-bridge sine wave inverter circuit. <https://www.homemade-circuits.com>
- Pefhany, S. (2011). Bootstrap capacitor selection with IR2110. <https://electronics.stackexchange.com/18423>
- Carpenter, T. (2015). IR2110 overheating discussion. <https://electronics.stackexchange.com/172414>
- Gupta, R., Bansal, S., & Jain, A. (2016). SPWM theory. <https://researchgate.net>